

# **PROJECT SIMULATION**

## **AUDIO AMPLIFIER (INDIVIDUAL COMPONENTS)**

### **TEAM**



YOGESH KRISHNA – 2024102035

ANUMAY RAI – 2025122013

TABLE NUMBER – 10


ROOM – N117

## Differential Circuit

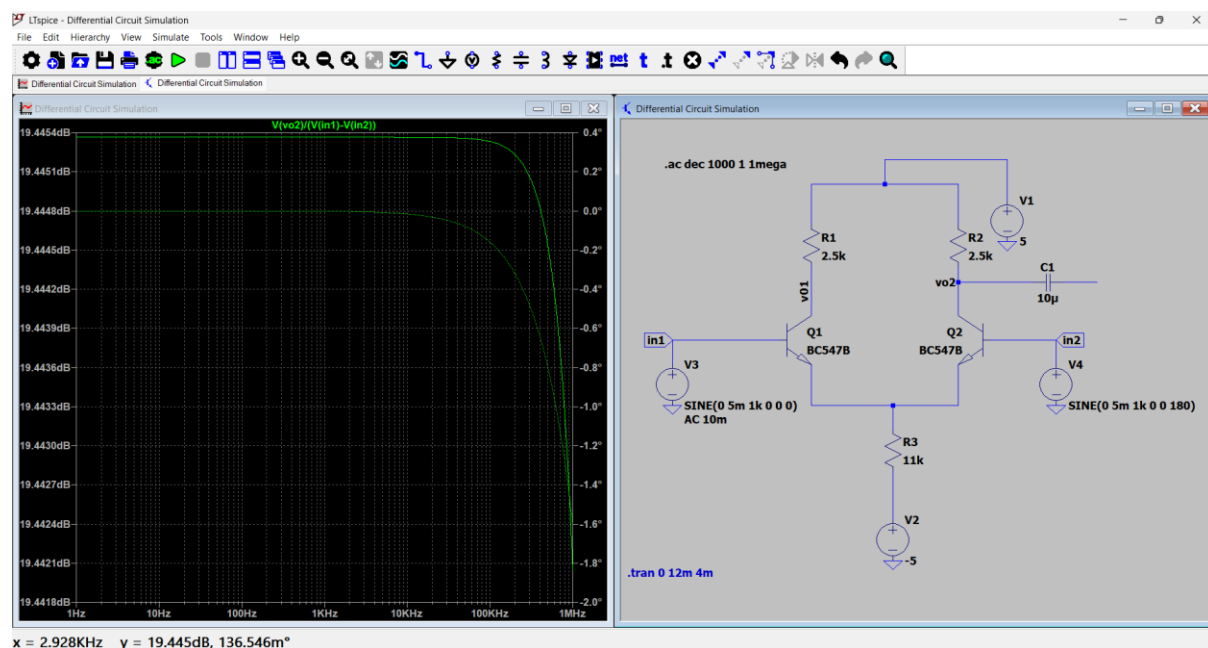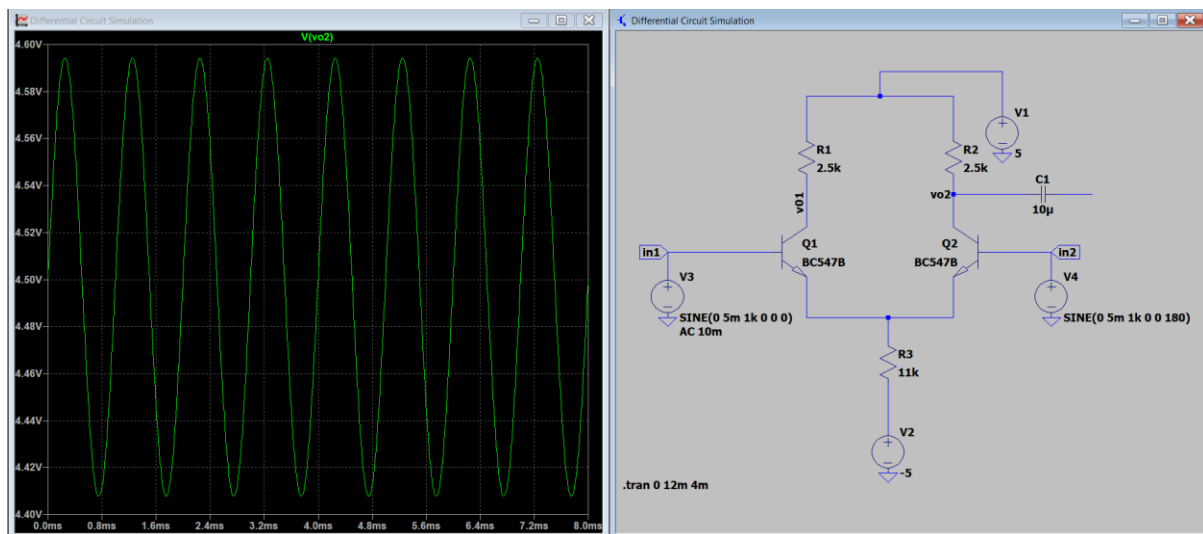


x = 2.928KHz y = 19.445dB, 136.546m°



## CE Amplifier

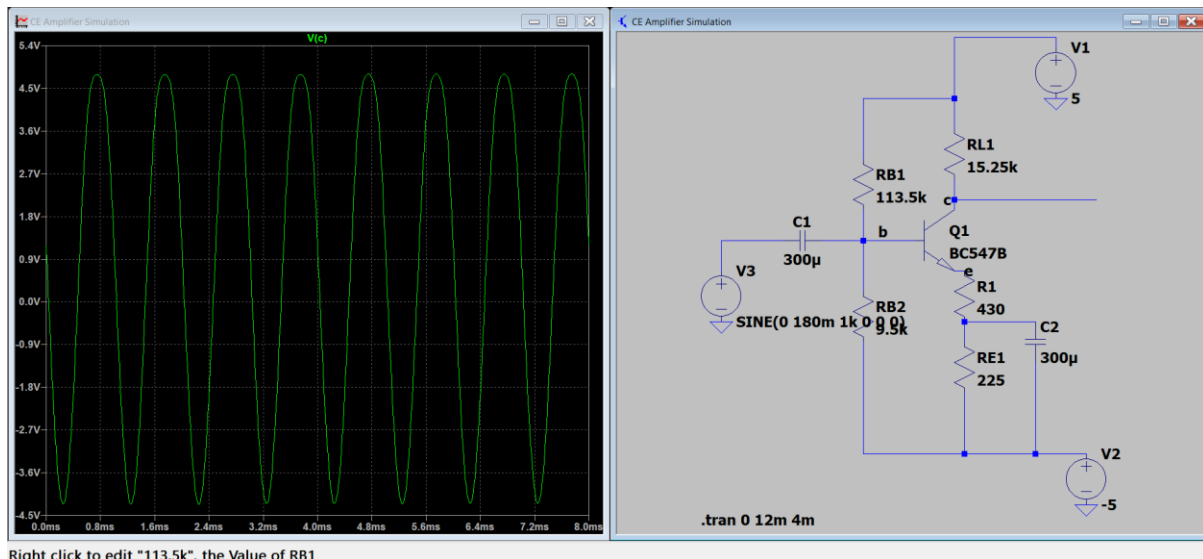


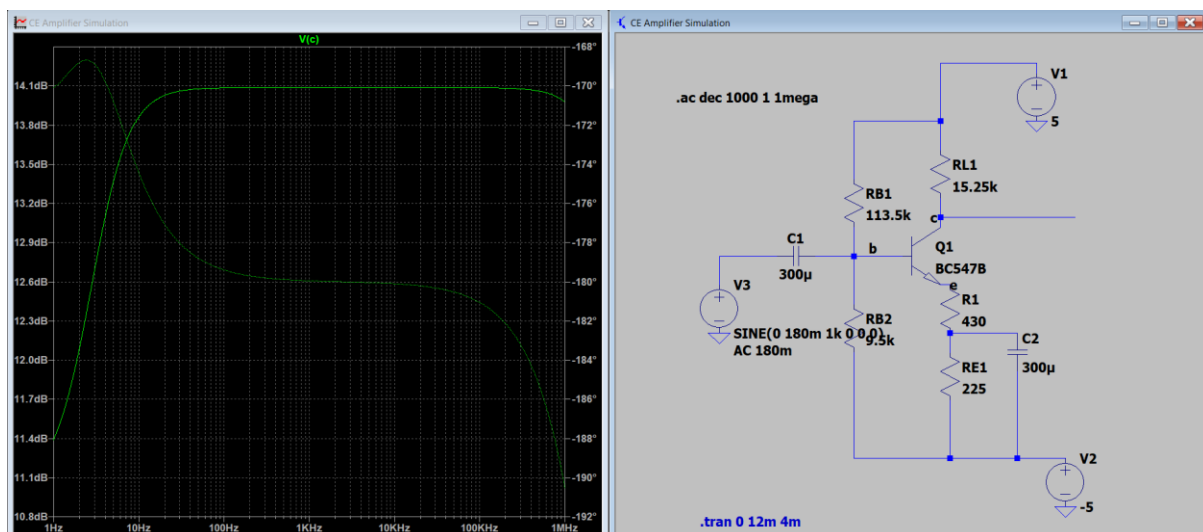
Right click to edit "113.5k", the Value of RB1



# Filter

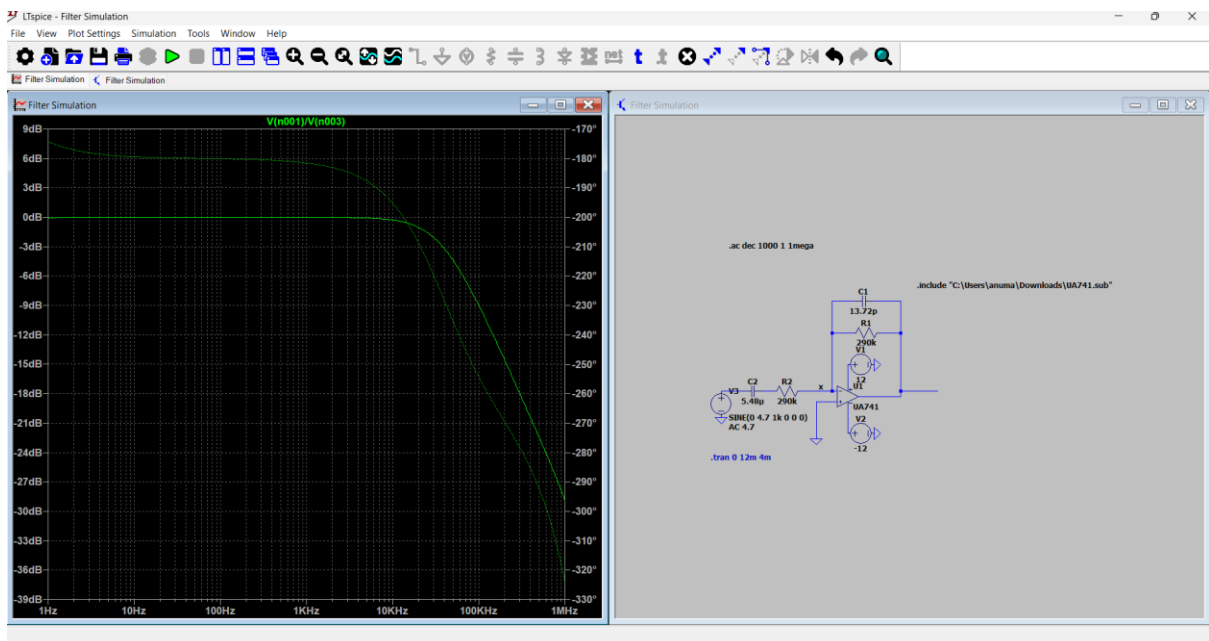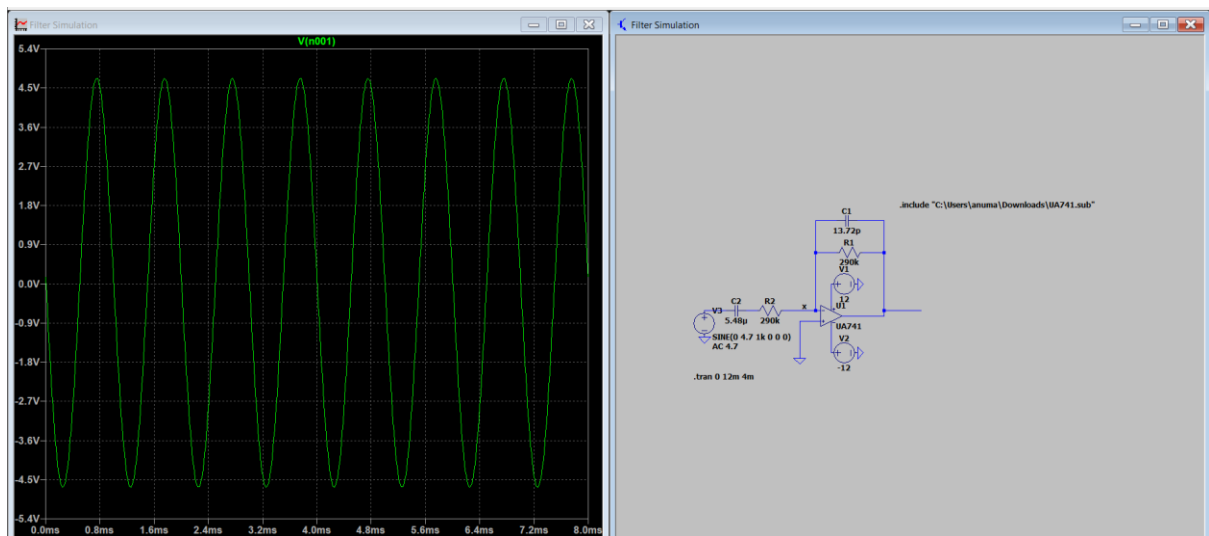

# Power Amplifier

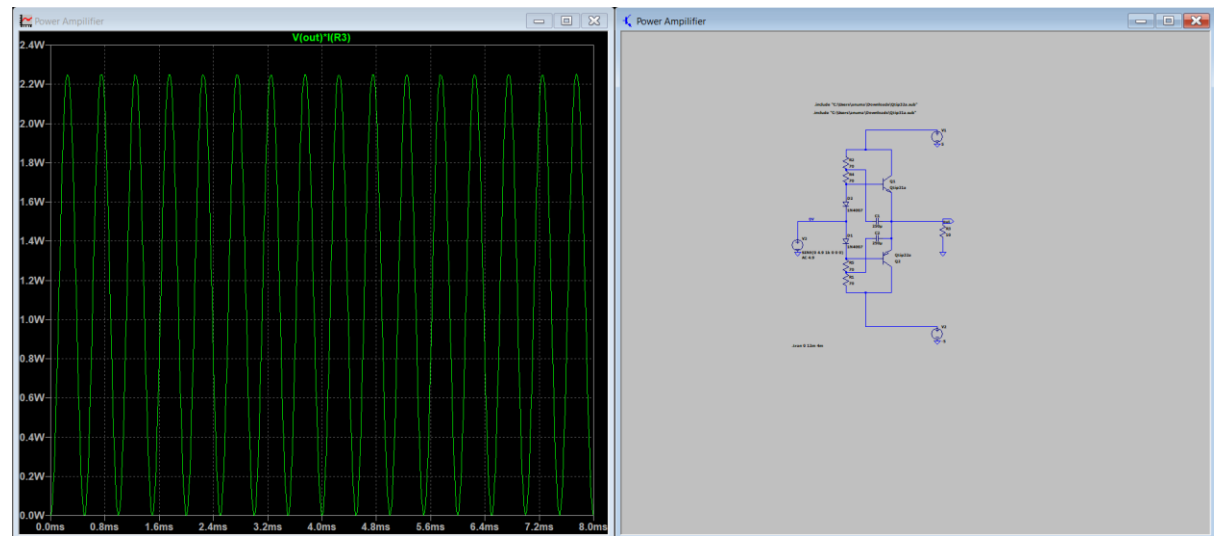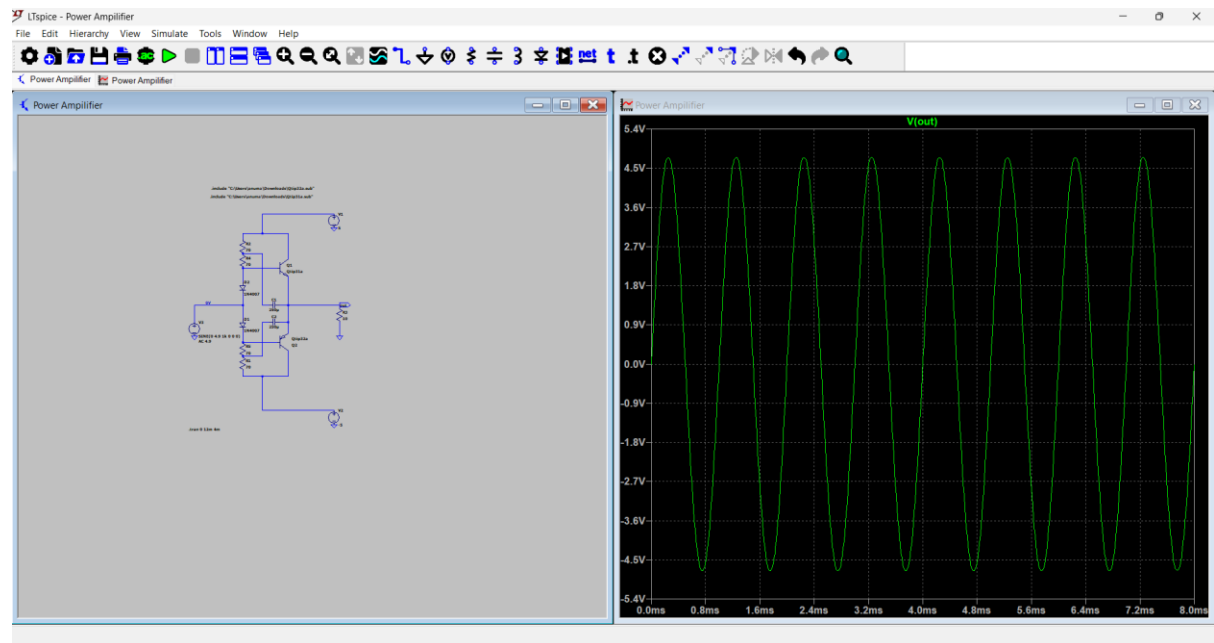

Open an existing document